



ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B

FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N
Prof. Vadhiraj K P P
Prof. Kruthika N
Prof. Suma S
Prof. Pushpa K R
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L
Prof. Dhanashree G Bhate
Dr. Renuka R Kajur
Prof. Rajesh Chandrashekar
Prof. Sangam Kumar G H


ELEMENTS OF ELECTRICAL ENGINEERING (UE25EE141A/B)

Analysis of Series RLC circuit ; Impedance and Power Triangles

Jyothi T N

Department of Electrical & Electronics Engineering

Series RLC Circuit

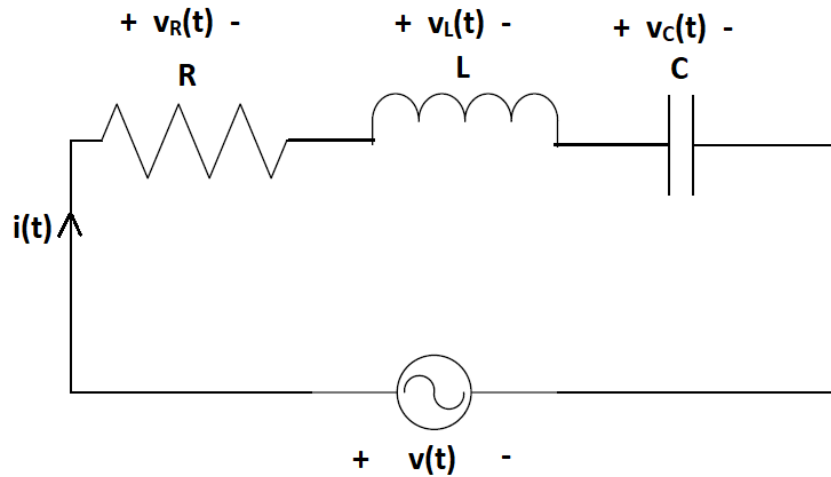

By KVL, $v(t) = v_R(t) + v_L(t) + v_C(t)$

In Phasor form, $\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$

$$\bar{V}_R = \bar{I} * R \quad \bar{V}_L = \bar{I} * (jX_L) \quad \bar{V}_C = \bar{I} * (-jX_C)$$

$$\bar{V} = \bar{I} * (R + jX_L - jX_C)$$

$$Z_T = \frac{\bar{V}}{\bar{I}} = (R + jX_L - jX_C) = \sqrt{R^2 + (X_L - X_C)^2} \angle \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$


Case 1: $X_L > X_C$

If $X_L > X_C$ then $IX_L > IX_C$

i.e., $|\overline{V}_L| > |\overline{V}_C|$

The circuit behaves effectively as inductive circuit i.e., series RL type.

Phasor Diagram:

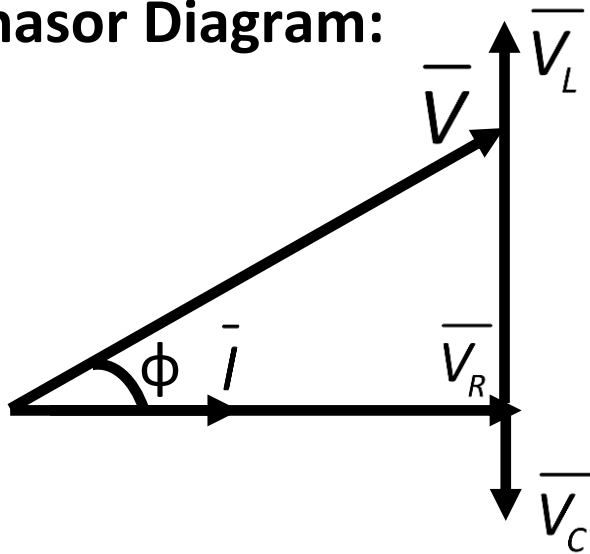

$$\begin{aligned}\phi &= \tan^{-1}\left(\frac{|\overline{V}_L| - |\overline{V}_C|}{|\overline{V}_R|}\right) = \tan^{-1}\left(\frac{V_L - V_C}{V_R}\right) \\ &= \tan^{-1}\left(\frac{X_L - X_C}{R}\right)\end{aligned}$$


Case 2: $X_C > X_L$

If $X_C > X_L$ then $IX_C > IX_L$

i.e., $|\overline{V_C}| > |\overline{V_L}|$

The circuit behaves effectively as a capacitive circuit i.e., series RC type.

Phasor Diagram:

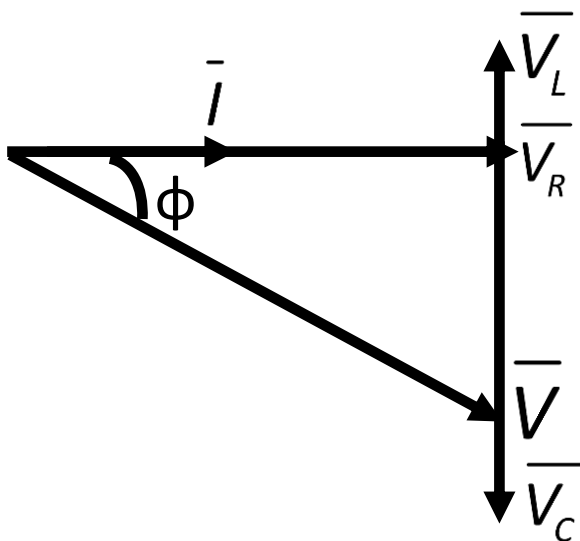

$$\phi = \tan^{-1}\left(\frac{|\overline{V_L}| - |\overline{V_C}|}{|\overline{V_R}|}\right) = \tan^{-1}\left(\frac{V_L - V_C}{V_R}\right)$$
$$= \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$


Note: ϕ will be negative in this case since $X_L < X_C$

Case 3: $X_L = X_C$

If $X_L = X_C$ then $IX_L = IX_C$ $|\overline{V}_L| = |\overline{V}_C|$

The circuit behaves effectively as a purely resistive circuit. This case is called '**Series Resonance**' case.

Phasor Diagram:

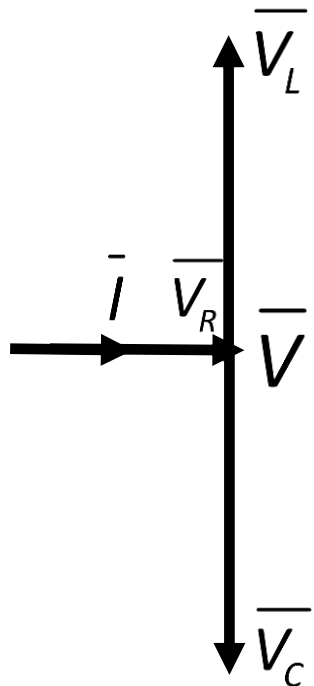

$$\overline{V} = \overline{V}_R$$


$$Z = R$$

$$\phi = 0^\circ$$


Impedance & Power Triangles – Series RLC Circuit

For a series RLC circuit, $Z = R + j(X_L - X_C) = \sqrt{R^2 + (X_L - X_C)^2} \angle \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$

Case i) $X_L > X_C$

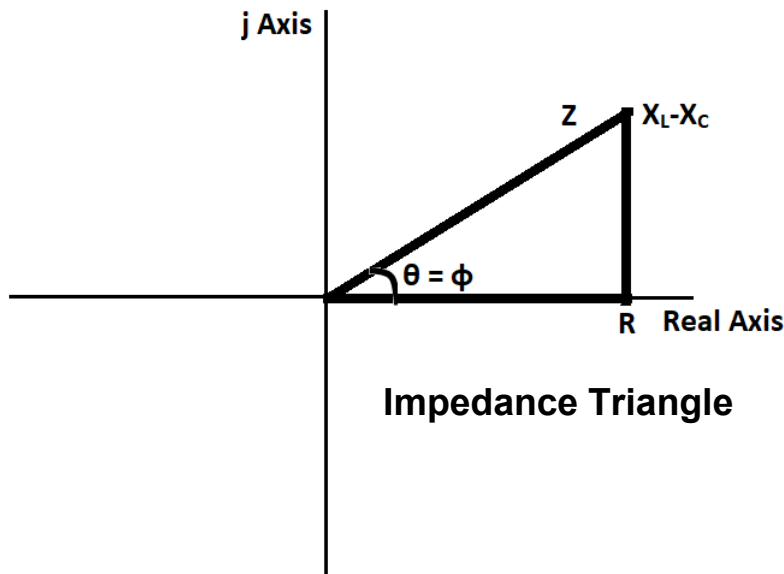

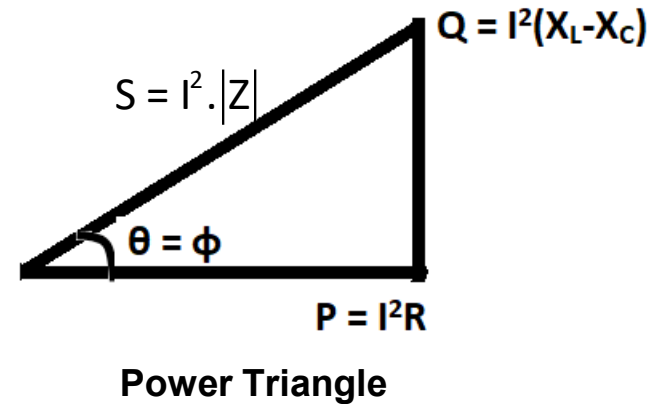Impedance Triangle of a series RLC circuit for $X_L > X_C$ lies in Quadrant I of complex plane.



$$P = VI \cos \phi = I^2 R$$

$$Q = VI \sin \phi = I^2 (X_L - X_C)$$

$$S = VI = I^2 |Z|$$

Text Book & References

Text Book:

1. **“Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017**
2. **“Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019**
3. **“Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014**

Reference Books:

1. **“Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023**
2. **“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.**



THANK YOU

Jyothi T.N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu