



ENGINEERING MATHEMATICS I

T R Geetha

Department of Science and Humanities

ENGINEERING MATHEMATICS I

HIGHER ORDER LINEAR DIFFERENTIAL EQUATIONS

T R Geetha

Department of Science and Humanities

ENGINEERING MATHEMATICS I

HIGHER ORDER LINEAR DIFFERENTIAL EQUATIONS



CLASS CONTENT:

- ❑ Applications of LDE to electric circuits


ENGINEERING MATHEMATICS I

LCR Circuits

RLC Circuit

A simple RLC circuit consists of an inductor of inductance ' L ' (in henries), a Capacitor of capacitance ' C ' (in farads) and a resistor of resistance ' R ' (in ohms) and a source of electromotive force $E(t)$ (in volts) are connected in series.

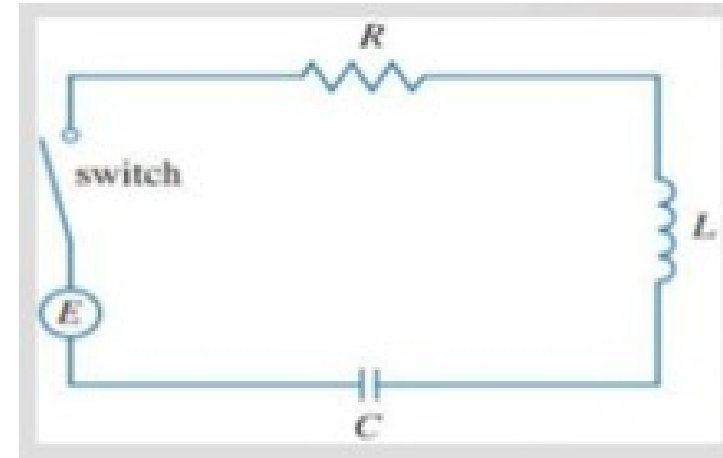The current ' I ' through the circuit is measured in amperes and the charge ' Q ' on the capacitor is measured in coulombs.



ENGINEERING MATHEMATICS I

LCR Circuits



The equation for the current $I(t)$ in the RLC circuit is obtained by considering the voltage drops across three components.

The voltage drop across the inductor is given by $E_L = L \frac{dI}{dt}$

The voltage drop across the resistor is given by $E_R = R I$

The voltage drop across the capacitor is given by $E_c = \frac{Q}{C}$

From Kirchhoff's Voltage Law,

The voltage supplied = The voltage drop across the
by the battery circuit components

***(the sum of these voltage
drops is equal to the electromotive force)***

ENGINEERING MATHEMATICS I

LCR Circuits



i.e, $E(t) = V_L + V_R + V_C$

$$E(t) = L \frac{dI}{dt} + R I + \frac{Q}{C}$$

'I' is the current in the entire circuit and 'Q' is the charge on the capacitor.

We know that, $I = \frac{dQ}{dt}$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = E(t)$$

This is the differential equation which describes LCR – Circuit.

ENGINEERING MATHEMATICS I

LCR Circuits



$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = E(t)$$

It is a second order linear differential equation with constant coefficients. If the charge and the current are known at zero time, we can get an expression for $Q(t)$ and $I(t)$.

ENGINEERING MATHEMATICS I

RLC - Circuits



Example: Find an expression for $I(t)$ in RLC - circuit with $R = 8$ ohms , $L = 2$ henry, $C = 0.1$ farad, which is connected to a source of voltage $E(t) = 10$ volts , assuming zero charge and zero current when $t = 0$.

Solution: The differential equation of RLC - circuit is

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = E(t)$$

Using the values of R , L , C and E from the given problem, we get

$$2 \frac{d^2Q}{dt^2} + 8 \frac{dQ}{dt} + \frac{Q}{0.1} = 10$$

$$2 \frac{d^2Q}{dt^2} + 8 \frac{dQ}{dt} + \frac{Q}{0.1} = 10$$
$$\Rightarrow \frac{d^2Q}{dt^2} + 4 \frac{dQ}{dt} + 5Q = 5$$

The above equation is a non homogeneous LDE of order 2 with constant coefficients.

To find CF :

Auxiliary Equation is

$$m^2 + 4m + 5 = 0$$

The roots are $m = -2 \pm i$

$$CF = e^{-2t} (c_1 \cos t + c_2 \sin t)$$

ENGINEERING MATHEMATICS I

LCR Circuits



To find PI

PI is given by,

$$PI = \frac{5}{D^2 + 4D + 5} = 1$$

∴ The general solution is $Q(t) = CF + PI$

$$\therefore Q(t) = e^{-2t} (c_1 \cos t + c_2 \sin t) + 1 \quad \text{-----(1)}$$

To find c_1 and c_2

Using the given initial conditions, $I(0) = 0$ and $Q(0) = 0$ eqn (1)

$$0 = e^{-2 \cdot 0} (c_1 \cos 0 + c_2 \sin 0) + 1$$

$$0 = 1 \cdot (c_1 \cdot 1 + c_2 \cdot 0) + 1$$

$$c_1 = -1 \text{ ----- (2)}$$

To find c_2

differentiate eqn (1) wrt 't' and then use the given initial conditions.

$$\therefore \frac{dQ}{dt} = e^{-2t} (c_1 (-\sin t) + c_2 (\cos t)) + (-2)e^{-2t} (c_1 (\cos t) + c_2 (\sin t))$$

ENGINEERING MATHEMATICS I

LCR Circuits



Using the value of C_1 , we get

$$\therefore \frac{dQ}{dt} = I(t) = e^{-2t} (\sin t + c_2 (\cos t)) + (-2)e^{-2t} (-1(\cos t) + c_2 (\sin t)) \text{ ----- (3)}$$

Given, $I(0) = 0$

$$0 = 1. (\sin 0 + c_2 (\cos 0)) + (-2)e^0 (-1(\cos 0) + c_2 (\sin 0))$$

$$\Rightarrow c_2 = -2$$

Using the values of c_1 and c_2 in (1), we get

$$\text{Thus, } Q(t) = e^{-2t} (-\cos t - 2.\sin t) + 1 \text{ and}$$

$$I(t) = 5 e^{-2t} \sin t$$



THANK YOU

T R Geetha

Department of Science and Humanities