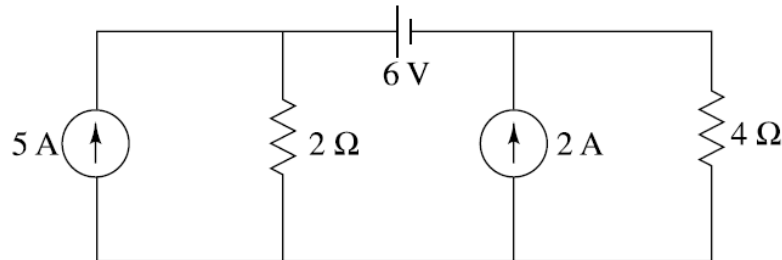



Unit I: DC Circuits

NOTES – CLASS 6


Q. Find the current in the 4Ω resistor using source transformation



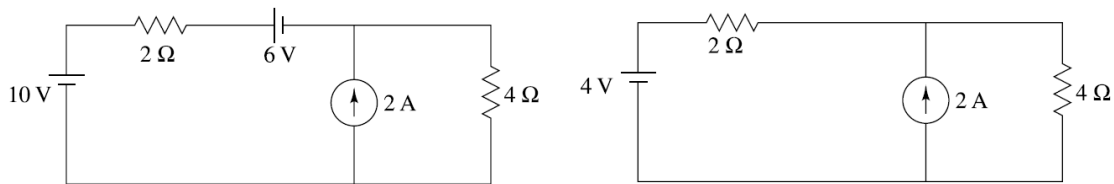Converting the parallel combination of the current source of 5 A and the resistor of 2Ω into an equivalent series combination of voltage source and resistor, we have



Again by source conversion,

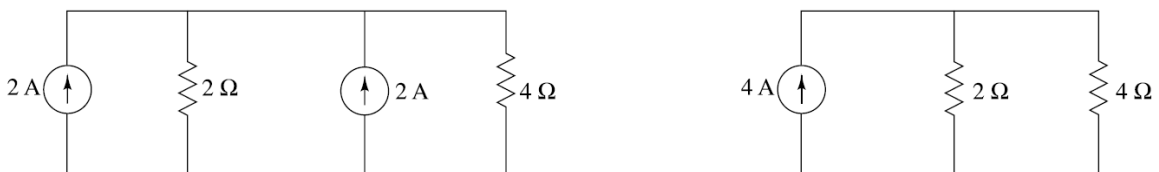

By current-division formula,

$$I_{4\Omega} = 4 \times \frac{2}{2+4} = 1.33 \text{ A}$$